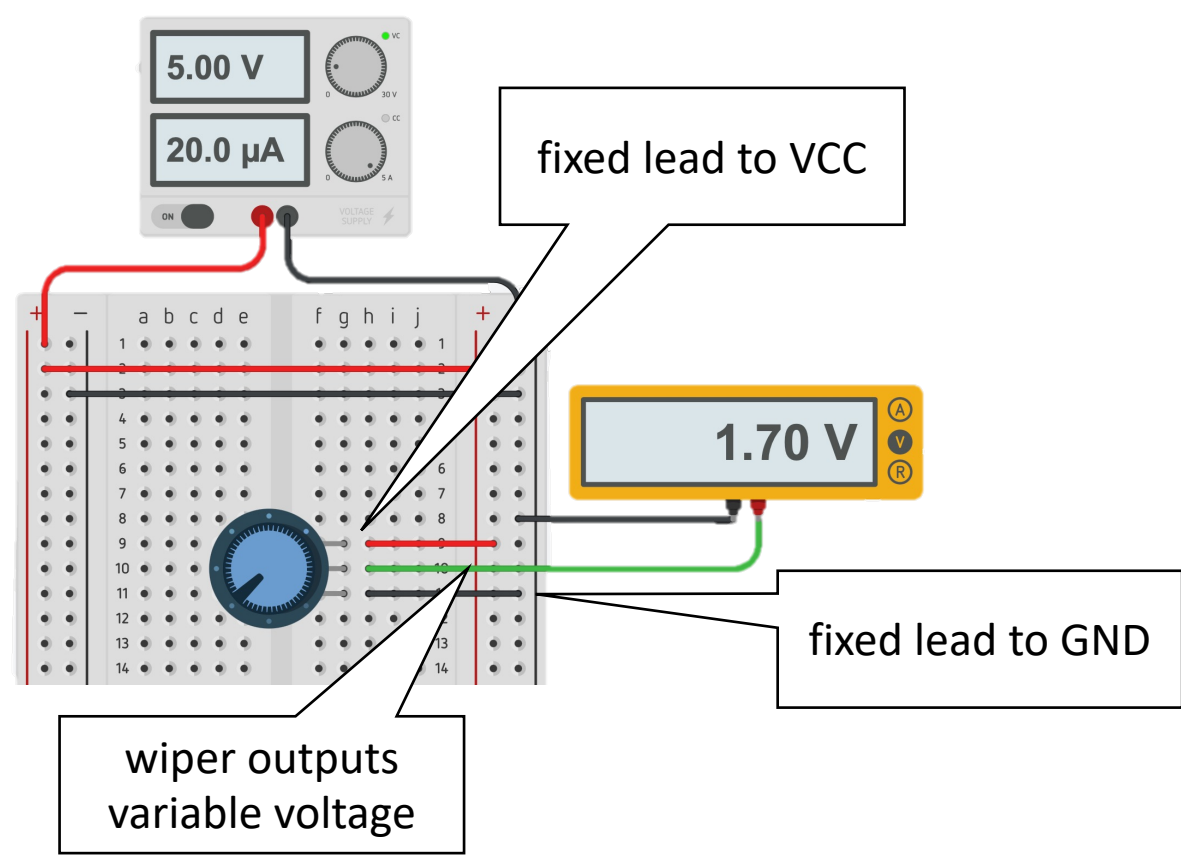


## Wiring as a potentiometer

Use when you need a variable voltage between VCC and GND.



## Wiring as a variable resistor

Use when you need a variable resistance.

